
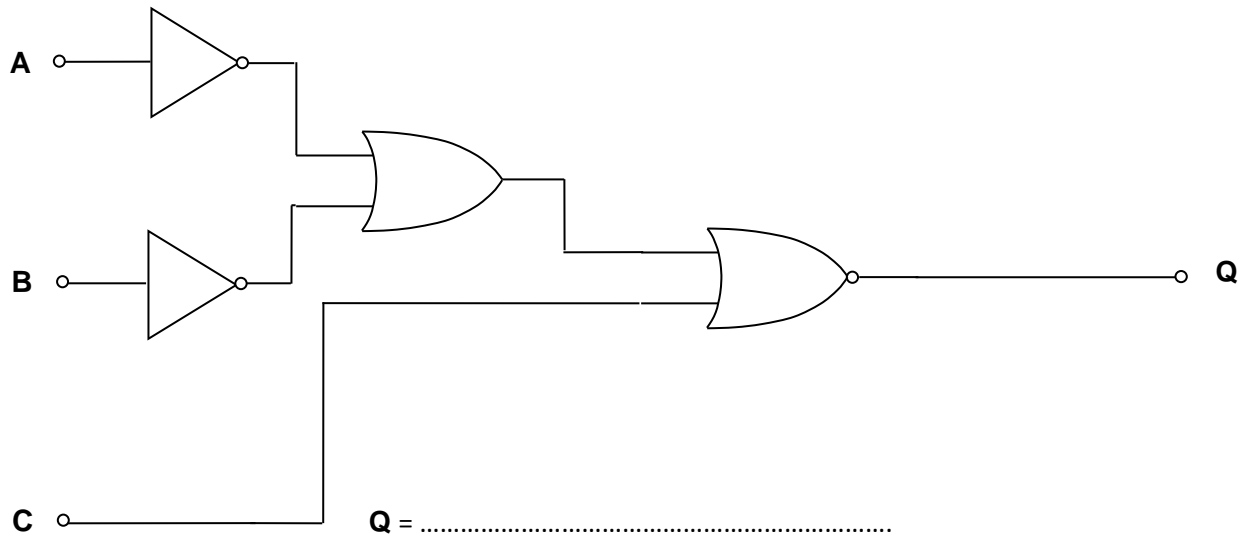


# Derive Boolean Expression from Logic Diagram


1.

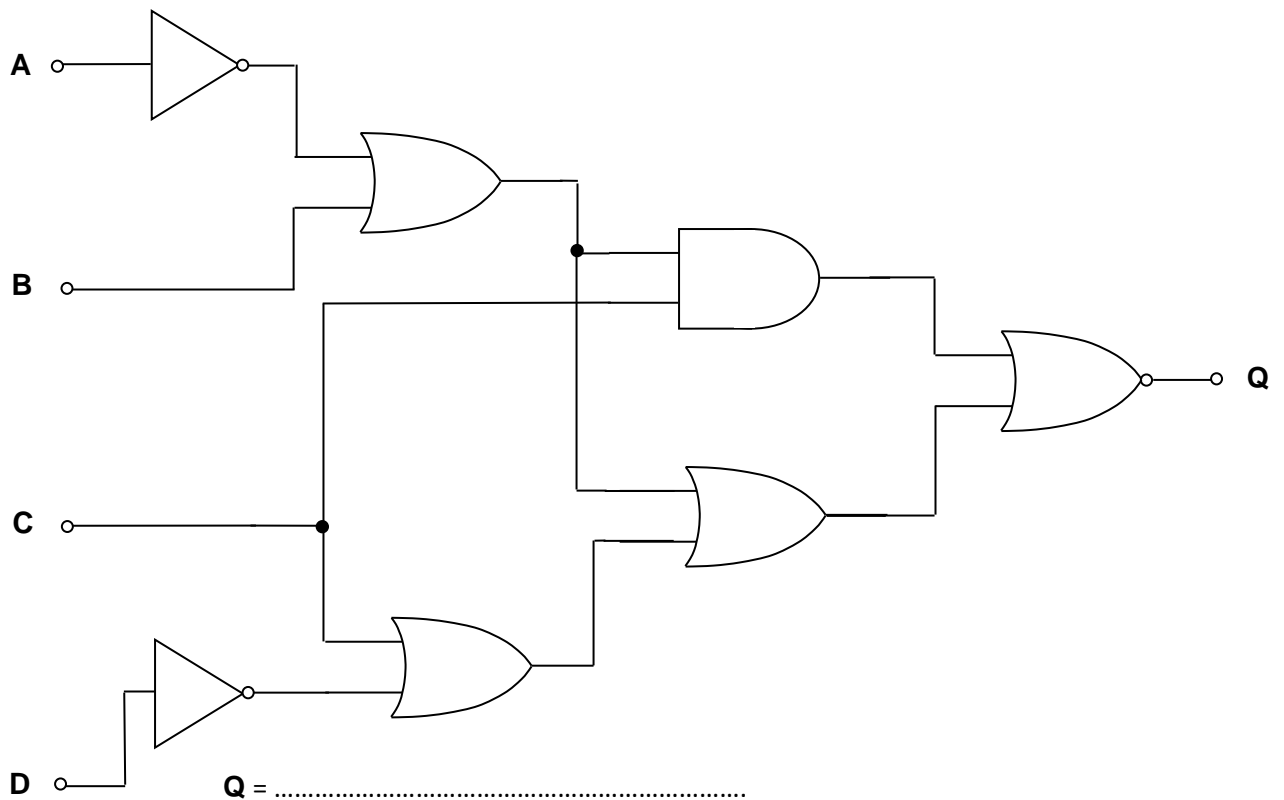

2.



3.

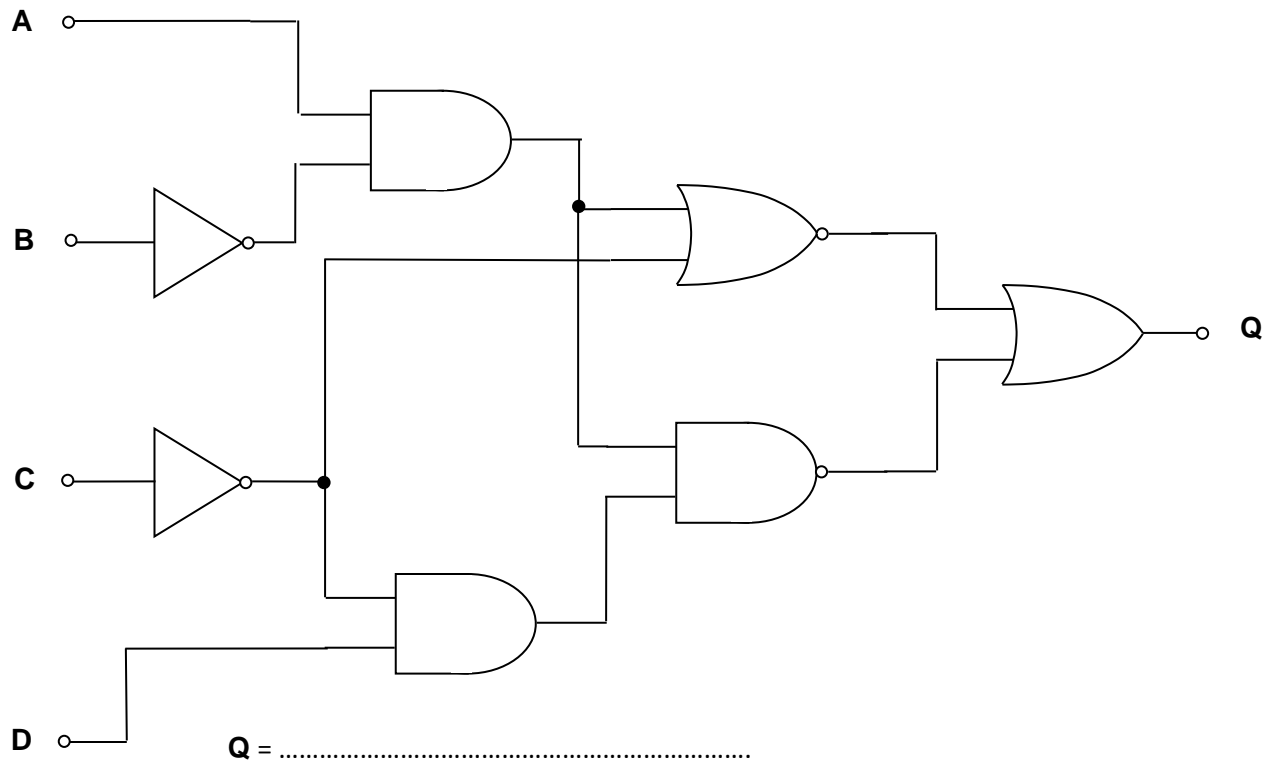

4.

